

# ECEN689: Special Topics in High-Speed Links Circuits and Systems Spring 2012

---

Lecture 3: Time-Domain Reflectometry & S-Parameter Channel Models



Sam Palermo  
Analog & Mixed-Signal Center  
Texas A&M University

# Announcements

---

- This Thursday lab time will be used for a make-up lecture
- No class next Monday
- Reference Material Posted on Website
  - TDR theory application note
  - S-parameter notes

# Agenda

---


- Interconnect measurement techniques
  - Time-domain reflectometry (TDR)
  - Network analyzer
- S-parameters
- Cascading S-parameter models
- Full S-parameter channel model
- Transient simulations
  - Impulse response generation
  - Eye diagrams
  - Inter-symbol interference

# Lecture References

---



- Majority of TDR material from Dally Chapter 3.4, 3.6 - 3.7
- Majority of s-parameter material from Hall "Advanced Signal Integrity for High-Speed Digital Designs" Chapter 9

# Interconnect Modeling

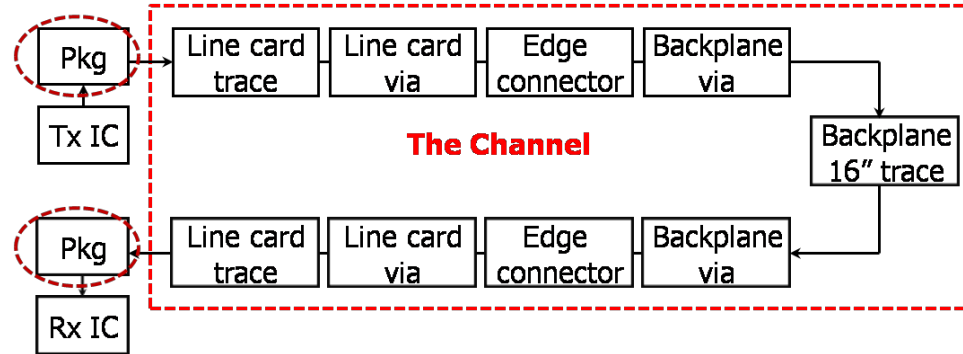


- Why do we need interconnect models?
  - Perform hand calculations and simulations (Spice, Matlab, etc...)
  - Locate performance bottlenecks and make design trade-offs
- Model generation methods
  - Electromagnetic CAD tools
  - Actual system measurements
- Measurement techniques
  - Time-Domain Reflectometer (TDR)
  - Network analyzer (frequency domain)

# Time-Domain Reflectometer (TDR)

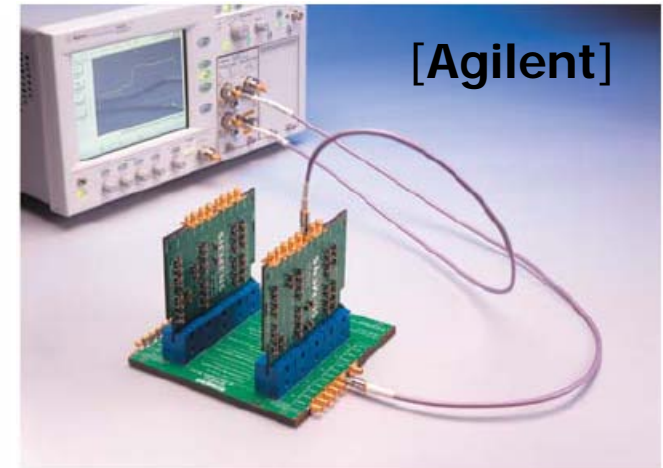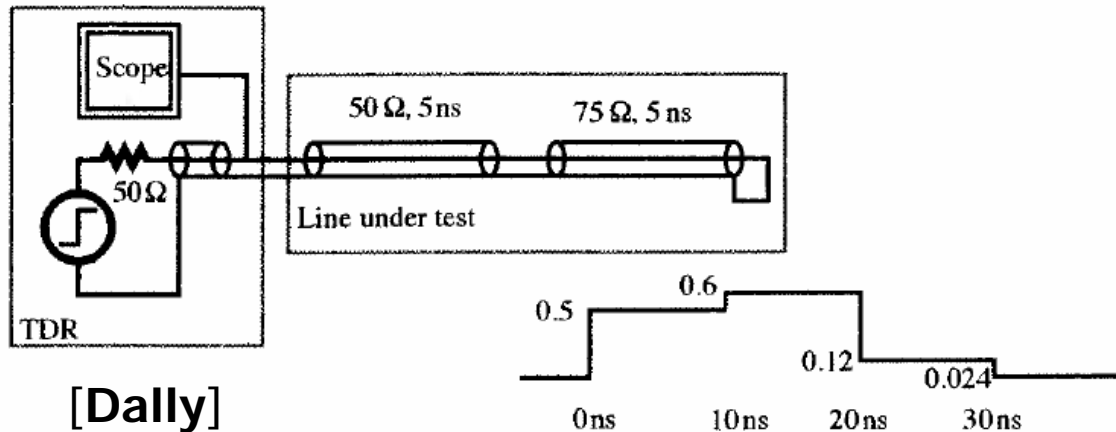

- TDR consists of a fast step generator and a high-speed oscilloscope
- TDR operation
  - Outputs fast voltage step onto channel
  - Observe voltage at source, which includes reflections
  - Voltage magnitude can be converted to impedance
  - Impedance discontinuity location can be determined by delay
- Only input port access to characterize channel

# TDR Impedance Calculation

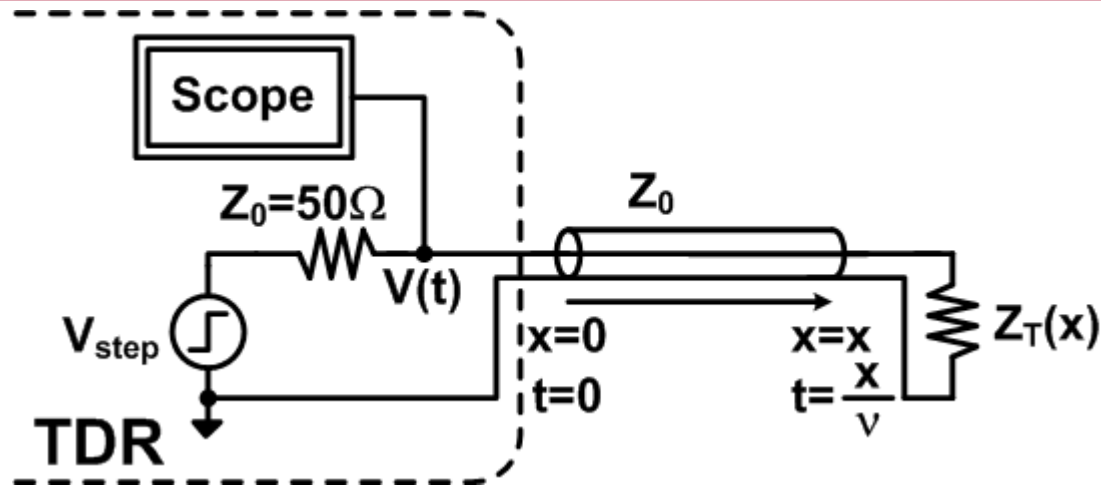

$$k_r(t) = \frac{V_r(t)}{V_i} = \frac{Z_T(t) - Z_0}{Z_T(t) + Z_0}$$



$$Z_T(t) = Z_0 \left( \frac{1 + k_r(t)}{1 - k_r(t)} \right) = Z_0 \left( \frac{V_i + V_r(t)}{V_i - V_r(t)} \right) = Z_0 \left( \frac{V(t)}{2V_i - V(t)} \right)$$

$$\text{If } V_{\text{STEP}} = 1V \Rightarrow V_i = 0.5V$$



$$\boxed{Z_T(t) = Z_0 \left( \frac{V(t)}{1V - V(t)} \right) \quad Z_T(x) = Z_T \left( t = \frac{2x}{v} \right)}$$

# TDR Waveforms (Open & Short)

- Open termination

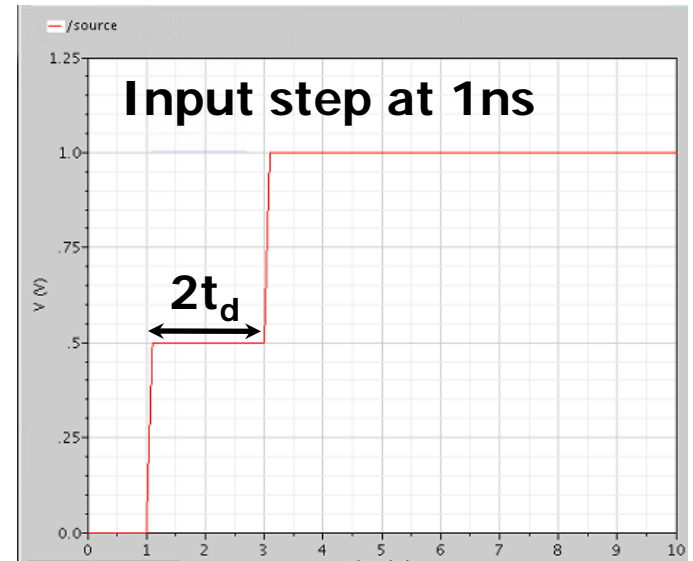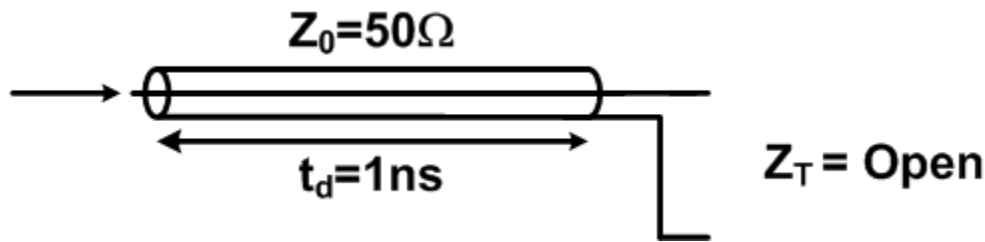



- Short termination

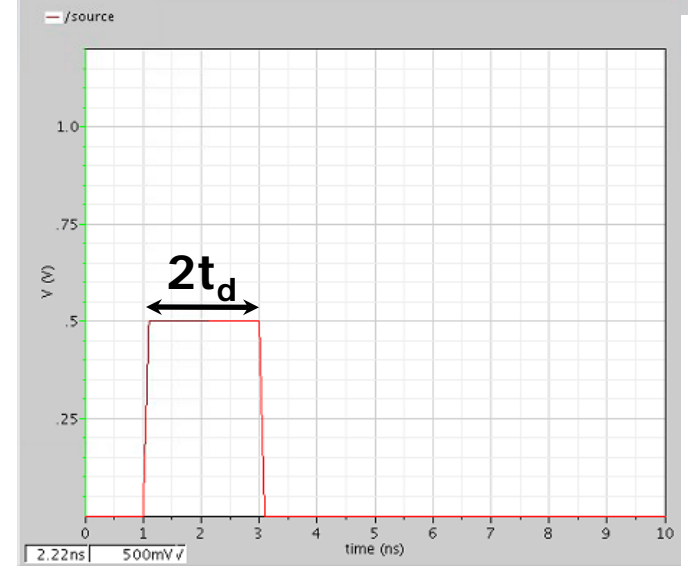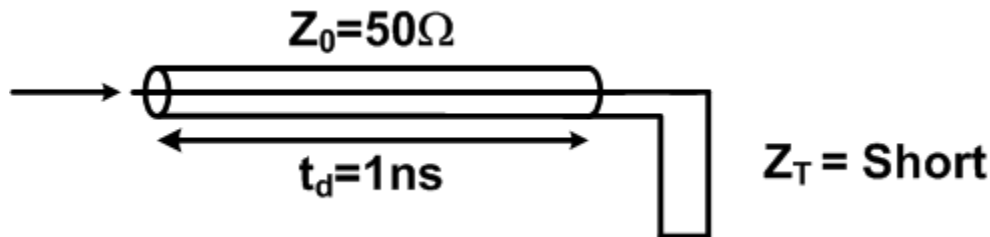





# TDR Waveforms (Matched & Mismatched)

- Matched termination

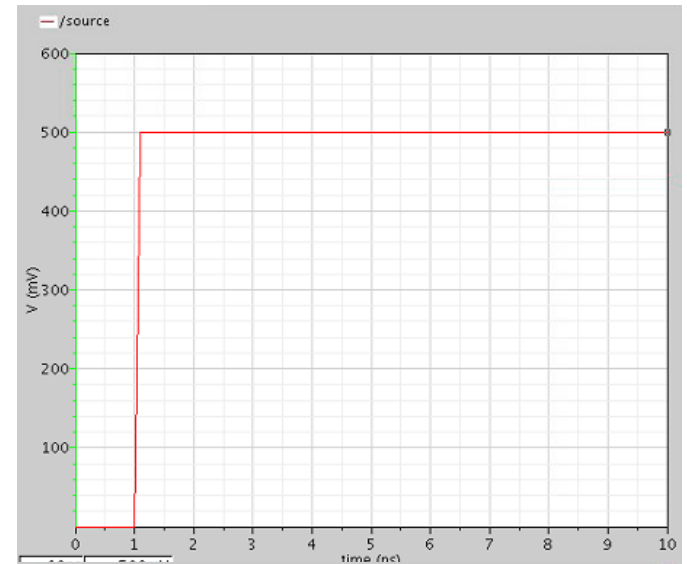
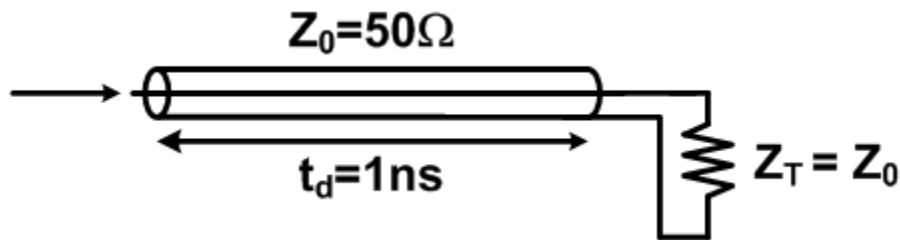


- Mismatched termination

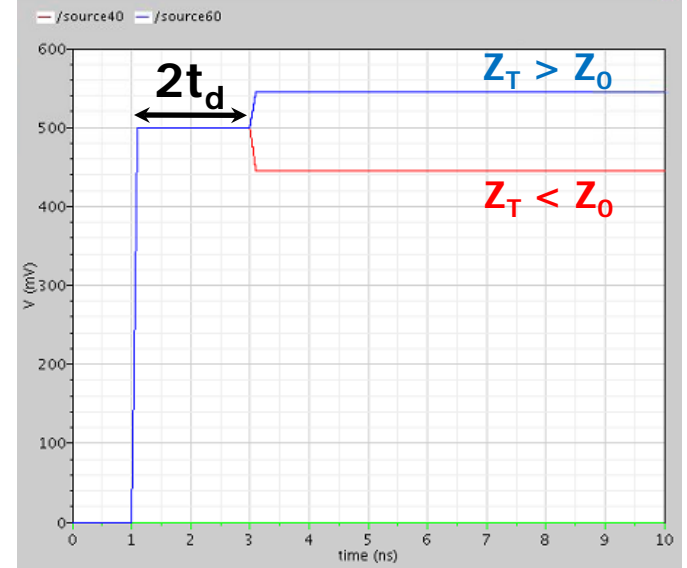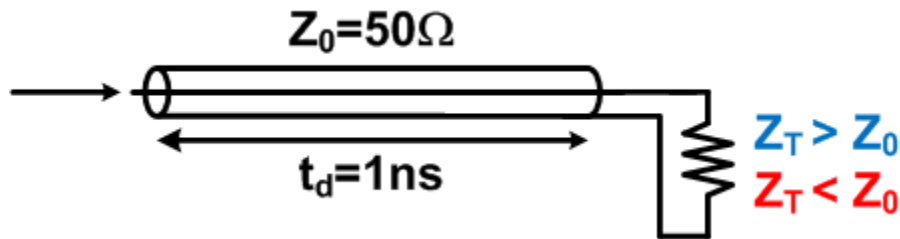


# TDR Waveforms (C & L Discontinuity)


- Shunt C discontinuity

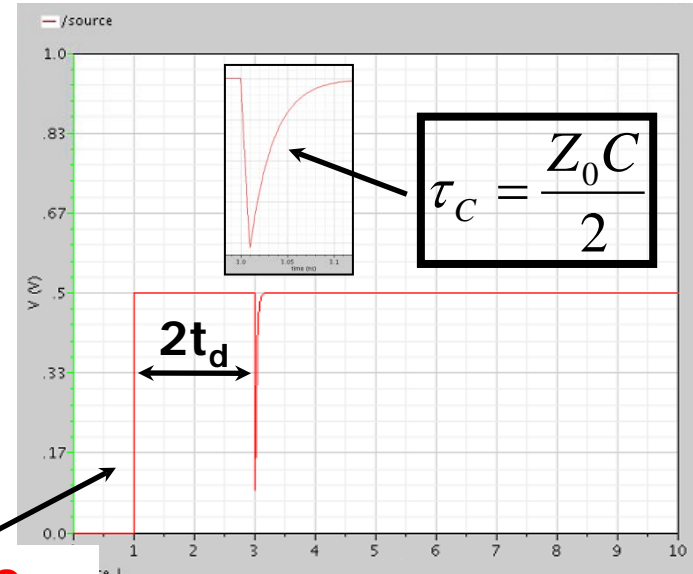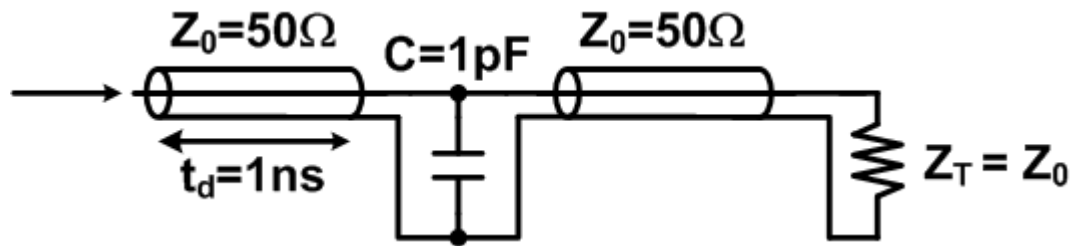

- Series L discontinuity

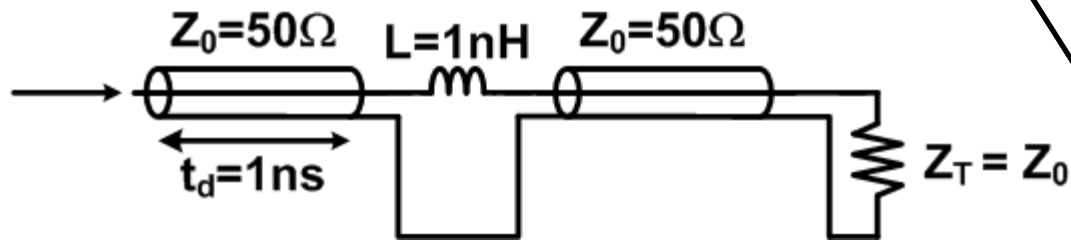

$t_r = 10\text{ps}$

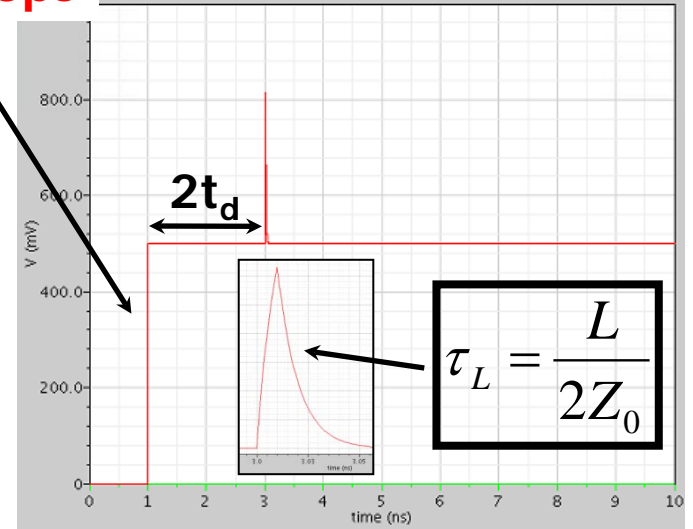

Peak voltage spike magnitude:

$$\frac{\Delta V}{V} = \left( \frac{\tau}{t_r} \right) \left[ 1 - e^{\left( -\frac{t_r}{\tau} \right)} \right]$$

# TDR Rise Time and Resolution



---

- TDR spatial resolution is set by step risetime



$$\Delta x > t_r v$$

- Step risetime degrades with propagation through channel
  - Dispersion from skin-effect
  - Lump discontinuities low-pass filter the step
- Causes difficulty in estimating L & C values
- Channel filtering can actually compensate for lump discontinuity spikes 😊


# TDR Multiple Reflections

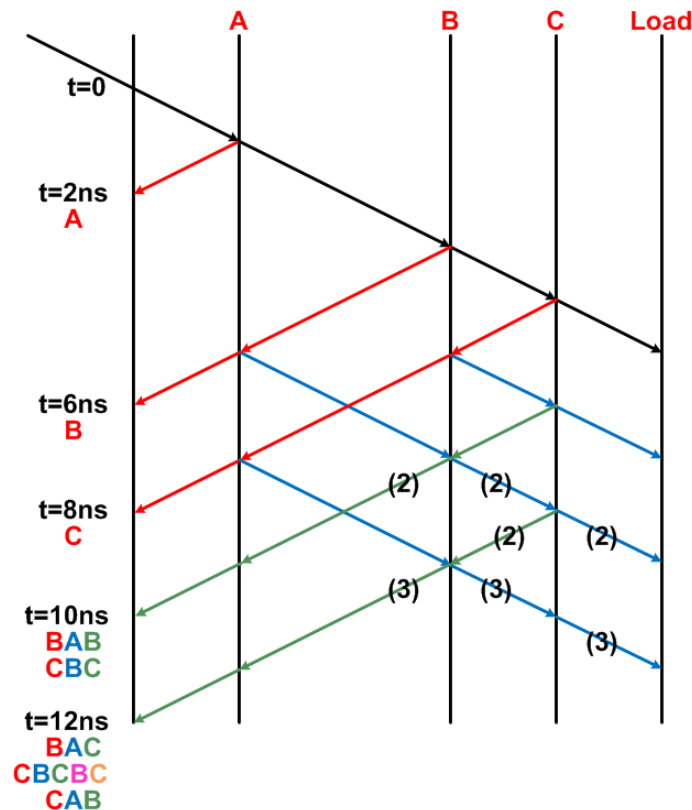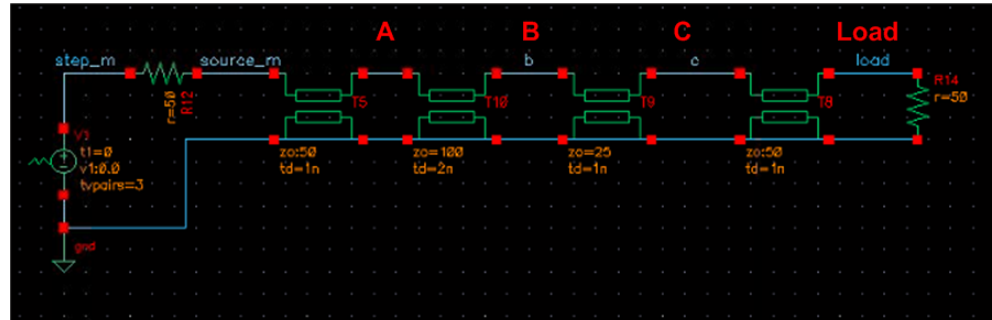
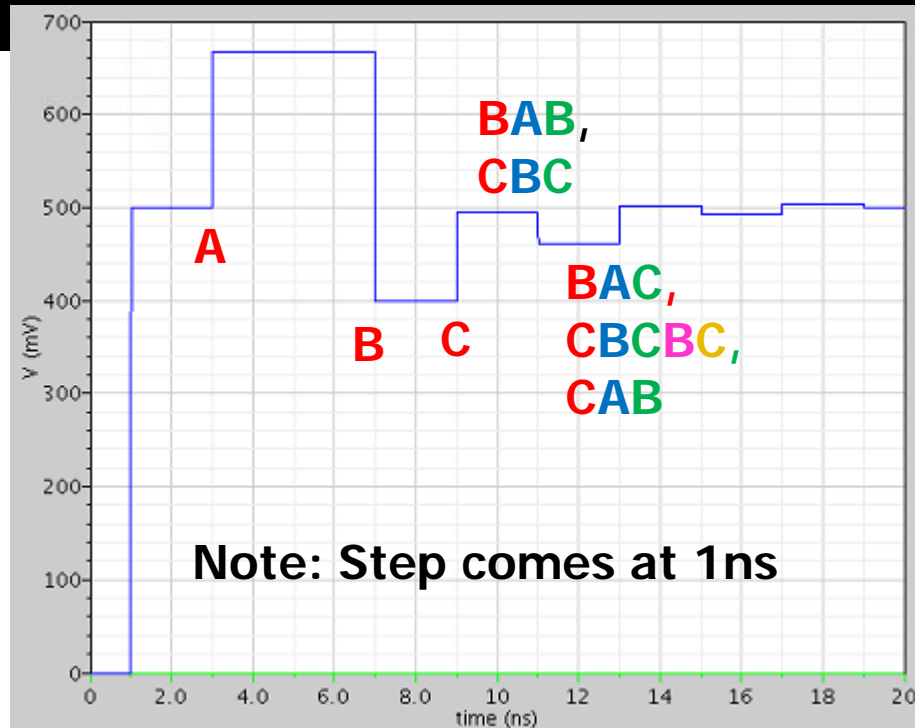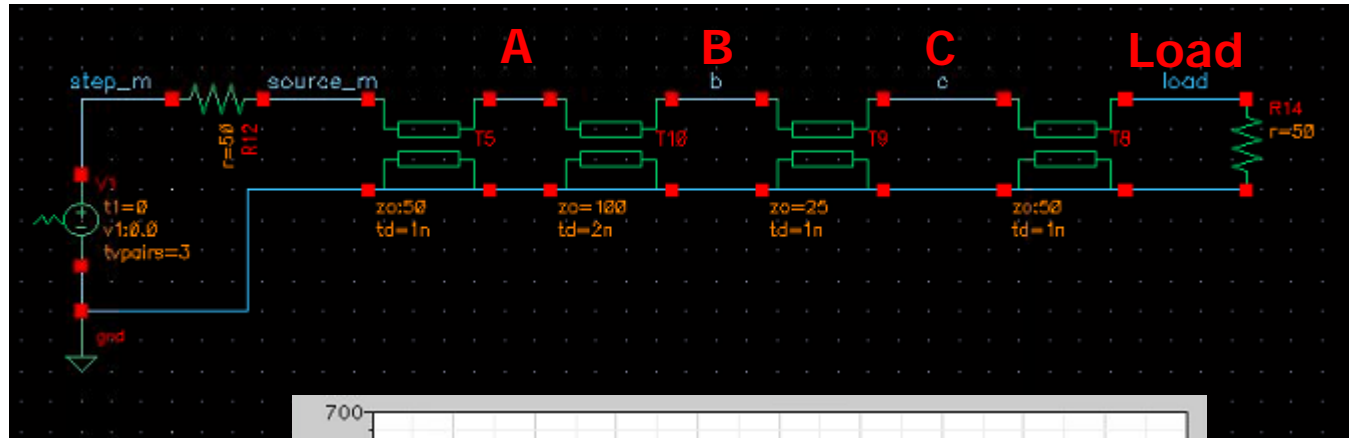
# TDR Waveforms (Multiple Discontinuities)





# Time-Domain Transmission (TDT)

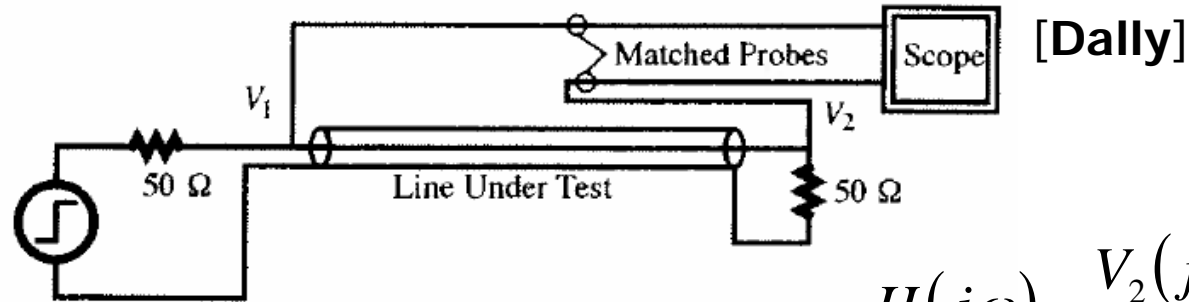


$$H(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)}$$

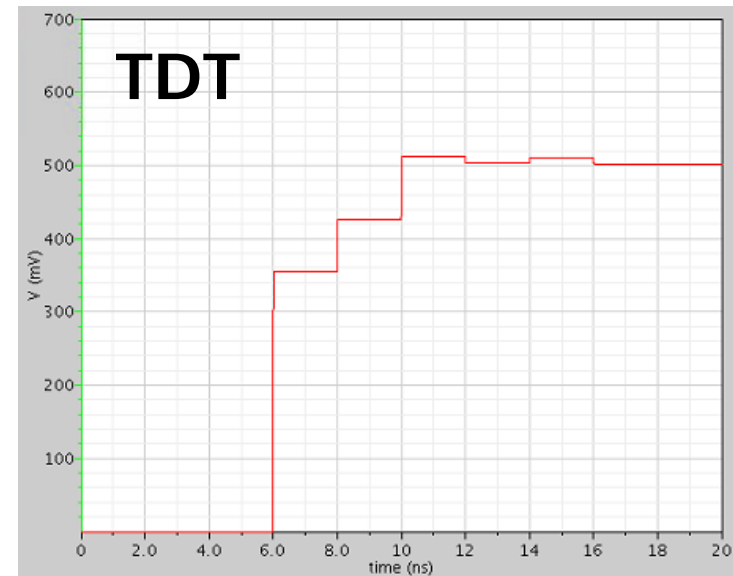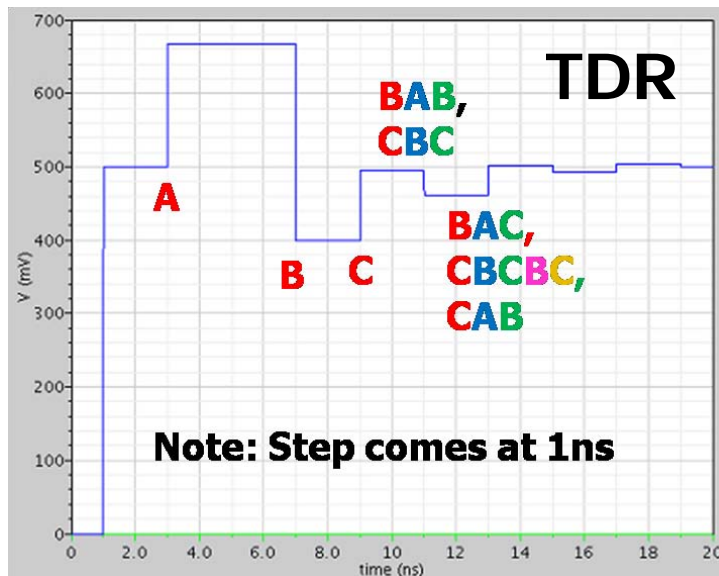- Can measure channel transfer function
- Hard to isolate impedance discontinuities, as they are superimposed on a single rising edge




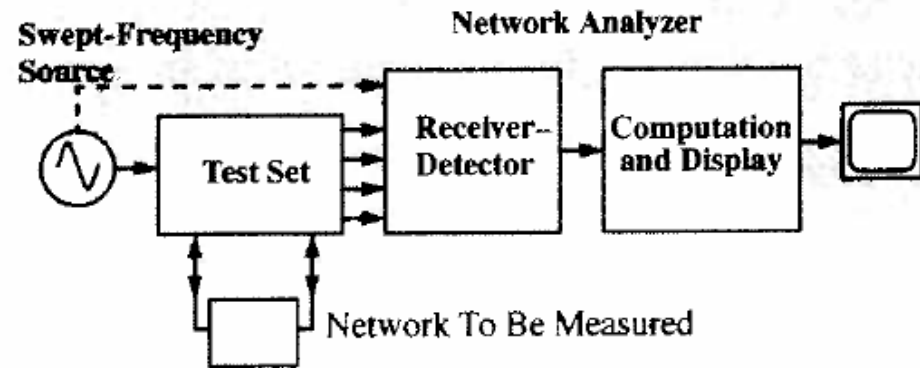
# Network Analyzer


- Stimulates network with swept-frequency source
- Measures network response amplitude and phase
- Can measure transfer function, scattering matrices, impedance, ...




[Dally]

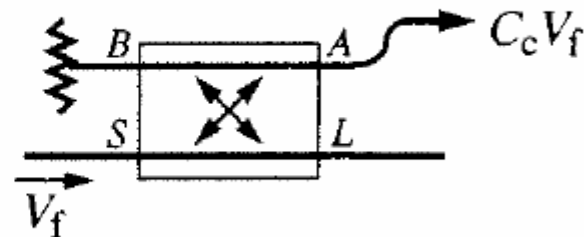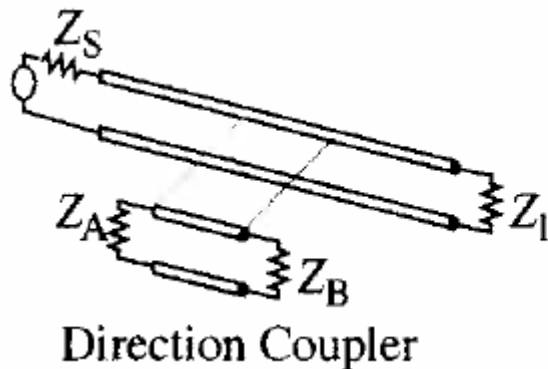
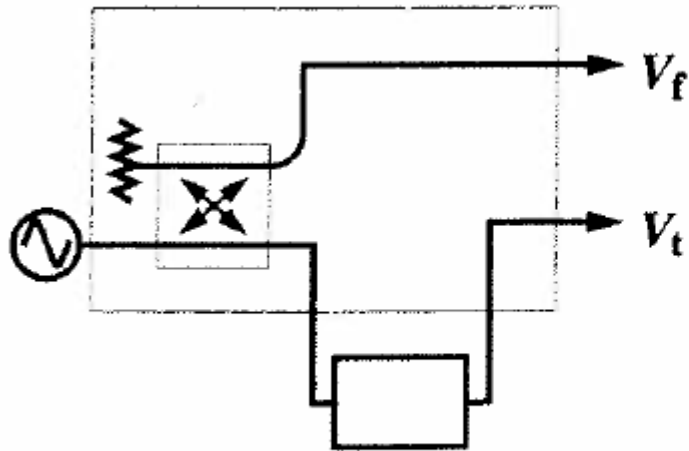
# Transfer Function & Impedance Measurements



Test Set for Transfer Function

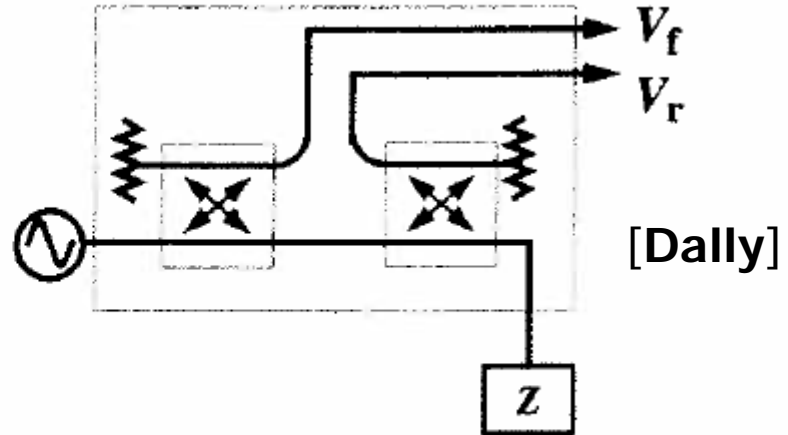


Test Set for Impedance Measurements


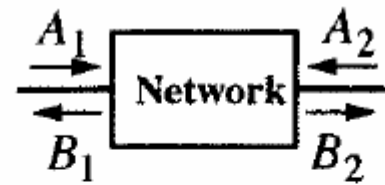
# Scattering (S) Parameters

---

- Why S Parameters?
  - Easy to measure
  - Y, Z parameters need open and short conditions
  - S parameters are obtained with nominal termination
  - S parameters based on incident and reflected wave ratio




The diagram shows a rectangular box labeled "Network". On the left side, there are two horizontal arrows: the top one points right and is labeled  $A_1$ , the bottom one points left and is labeled  $B_1$ . On the right side, there are two horizontal arrows: the top one points left and is labeled  $A_2$ , the bottom one points right and is labeled  $B_2$ .

$$\begin{bmatrix} B_1 \\ B_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \cdot \begin{bmatrix} A_1 \\ A_2 \end{bmatrix}$$

S-matrix [Dally]

# Formal S-Parameter Definitions

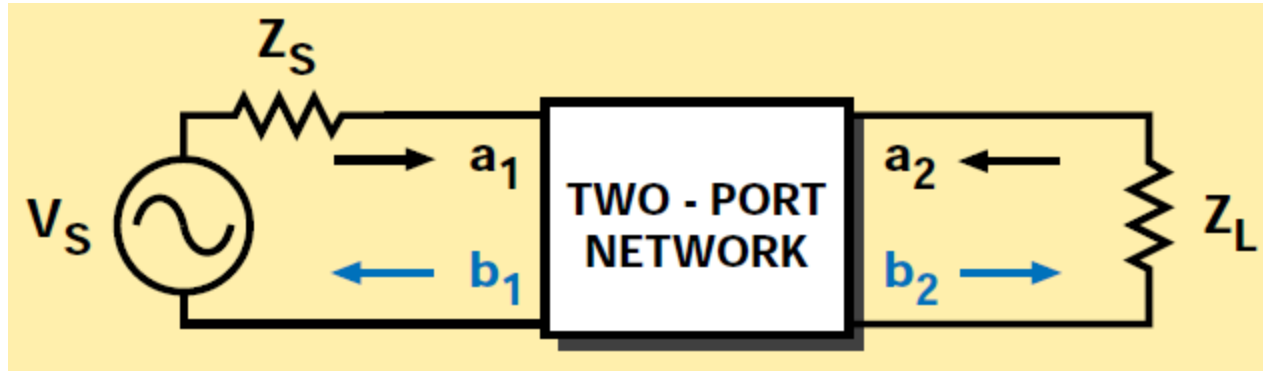

[Agilent]

$$s_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} = \text{Input reflection coefficient with the output port terminated by a matched load } (Z_L = Z_0 \text{ sets } a_2=0)$$

$$s_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0} = \text{Output reflection coefficient with the input terminated by a matched load } (Z_S = Z_0 \text{ sets } V_S=0)$$

$$s_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} = \text{Forward transmission (insertion) gain with the output port terminated in a matched load.}$$


$$s_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0} = \text{Reverse transmission (insertion) gain with the input port terminated in a matched load.}$$

# Cascading S-Parameters

---

- Network analysis allows cascading of independently characterized structures
- However, can't directly cascade s-parameter matrices and multiply
- Must first convert to an ABCD matrix (or T matrix)

# ABCD Parameters

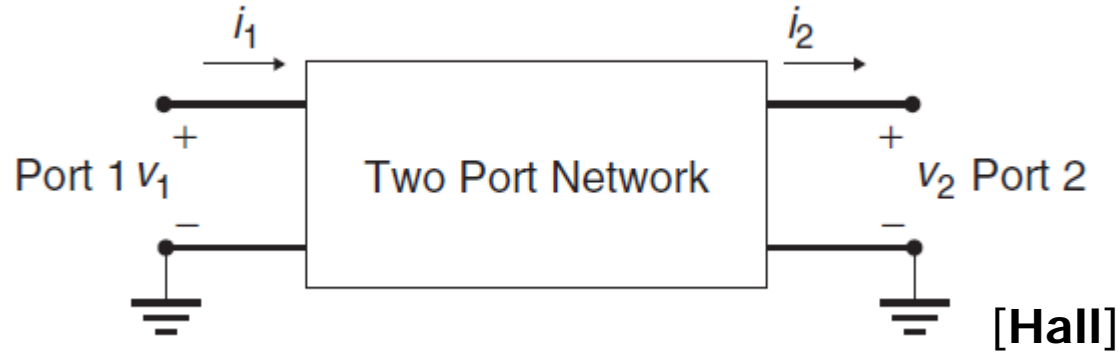

$$A = \left. \frac{v_1}{v_2} \right|_{i_2=0} \quad B = \left. \frac{v_1}{i_2} \right|_{v_2=0} \quad C = \left. \frac{i_1}{v_2} \right|_{i_2=0} \quad D = \left. \frac{i_1}{i_2} \right|_{v_2=0}$$

$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \bullet \begin{bmatrix} v_2 \\ i_2 \end{bmatrix}$$

# Converting Between S & ABCD Parameters

**TABLE 9-3. Relationships Between Two-Port  $S$  and  $ABCD$  Parameters<sup>a</sup>**


$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \quad \begin{bmatrix} \frac{B - Z_n(D - A + CZ_n)}{B + Z_n(D + A + CZ_n)} & \frac{2Z_n(AD - BC)}{B + Z_n(D + A + CZ_n)} \\ \frac{2Z_n}{B + Z_n(D + A + CZ_n)} & \frac{B - Z_n(A - D + CZ_n)}{B + Z_n(D + A + CZ_n)} \end{bmatrix}$$
  

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} \quad \begin{bmatrix} \frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{2S_{21}} & Z_n \frac{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}{2S_{21}} \\ \frac{1}{Z_n} \frac{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}{2S_{21}} & \frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{2S_{21}} \end{bmatrix}$$

<sup>a</sup> $Z_n$  is the termination impedance at the ports.

[Hall]
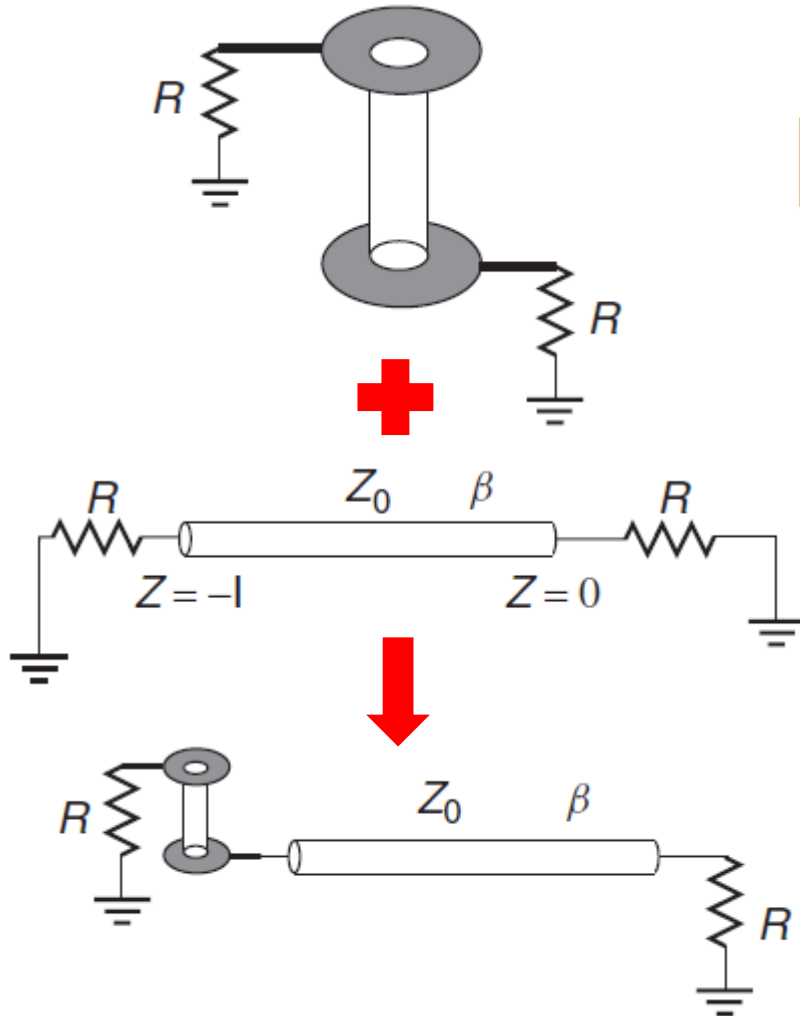
# Example: Cascaded Via & Transmission Line



$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}_{\text{via}} = \begin{bmatrix} -0.1235 - j0.1516 & 0.7597 - j0.6190 \\ 0.7597 - j0.6190 & -0.1235 - j0.1516 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_{\text{via}} = \begin{bmatrix} 0.790 & j22.22 \\ j0.01686 & 0.790 \end{bmatrix}$$


$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}_{\text{t-line}} = \begin{bmatrix} 0.00325 - j0.00323 & -1.00 - j0.003 \\ -1.00 - j0.003 & 0.00325 - j0.00323 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_{\text{t-line}} = \begin{bmatrix} -1 & j0.3228 \\ j0.000129 & -1 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_{\text{cascade}} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}_{\text{via}} \begin{bmatrix} A & B \\ C & D \end{bmatrix}_{\text{t-line}}$$

- Taken from "Advanced Signal Integrity for High-Speed Digital Designs" by Hall
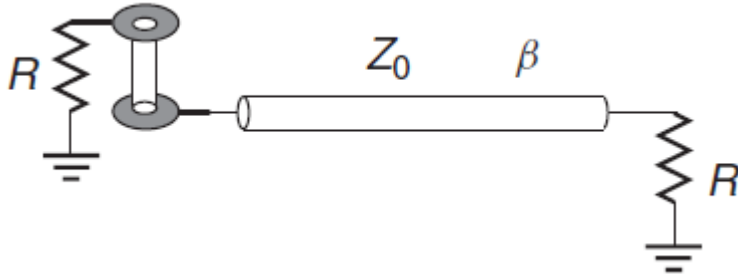
# Example: Cascaded Via & Transmission Line




$$\begin{aligned} \begin{bmatrix} A & B \\ C & D \end{bmatrix}_{\text{cascade}} &= \begin{bmatrix} A & B \\ C & D \end{bmatrix}_{\text{via}} \begin{bmatrix} A & B \\ C & D \end{bmatrix}_{\text{t-line}} \\ &= \begin{bmatrix} 0.790 & j22.22 \\ j0.01686 & 0.790 \end{bmatrix} \cdot \begin{bmatrix} -1 & j0.3228 \\ j0.000129 & -1 \end{bmatrix} \\ &= \begin{bmatrix} -0.790 & -j21.965 \\ -j0.01686 & -0.795 \end{bmatrix} \end{aligned}$$

- Using conversion table:

$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}_{\text{cascade}} = \begin{bmatrix} -0.1259 - j0.1553 & -0.7635 + j0.6186 \\ -0.7645 + j0.6182 & -0.1200 - j0.1565 \end{bmatrix}$$

- Can also use T matrixes to cascade
- Taken from "Advanced Signal Integrity for High-Speed Digital Designs" by Hall

# S-Parameter Channel Example

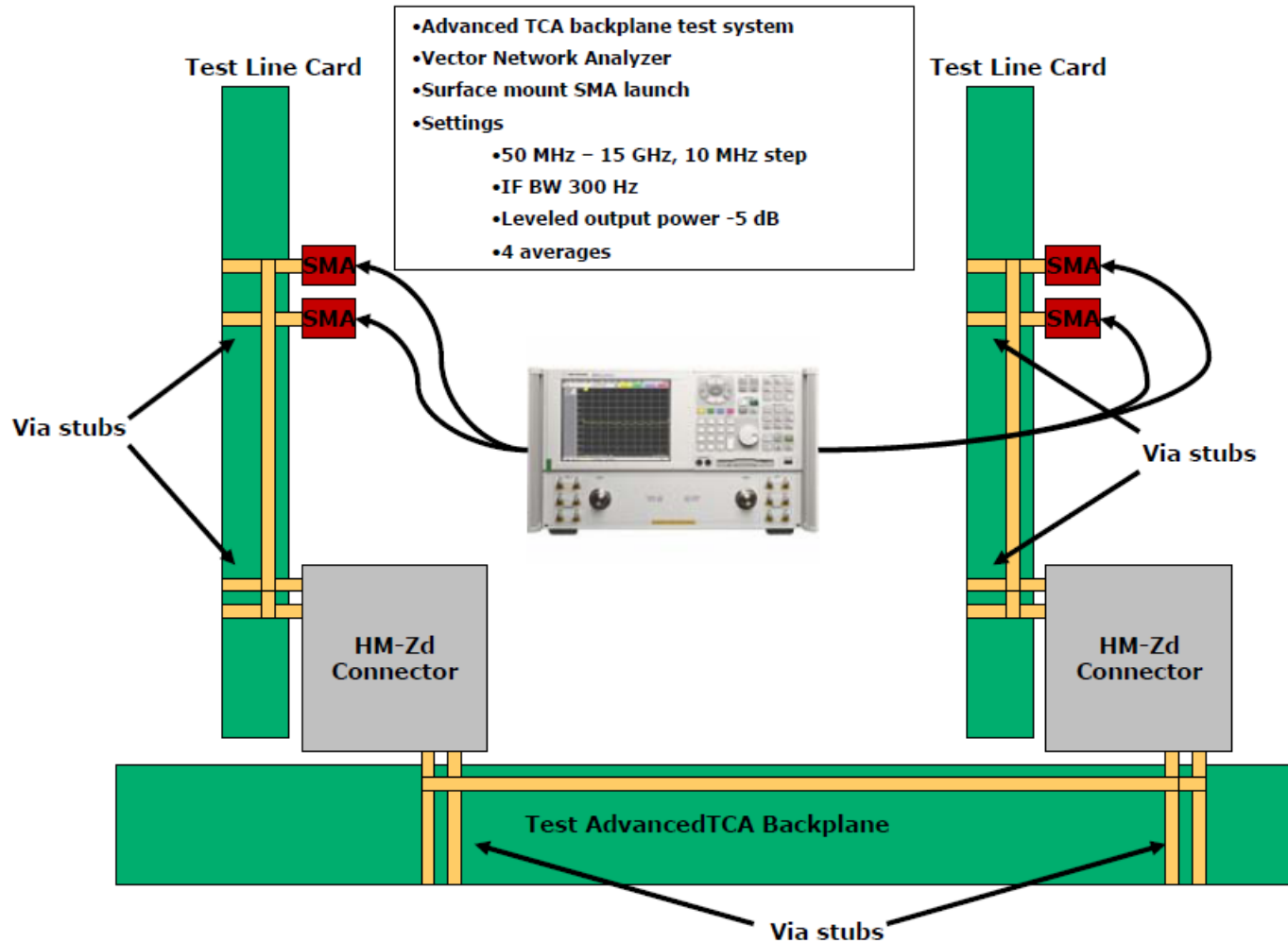

[Peters, IEEE Backplane Ethernet Task Force]




# S-Parameter Channel Example (4-port differential)

```
! peters_01_0605 rzo channel thru response
#      HZ      S      RI      R      50
!
! FREQ      S11      S12      S13      S14
!      S21      S22      S23      S24
!      S31      S32      S33      S34
!      S41      S42      S43      S44
!
!      REAL      IMAG      REAL      IMAG      REAL      IMAG      REAL      IMAG
5.00000000e+007  6.279266901548e-002 -5.256007502766e-002 -1.995363973143e-001 -9.018006169275e-001  7.405252014369e-002 -1.653914717779e-002  4.694410796534e-004  2.855671737566e-003
-1.993592781969e-001 -9.017752677900e-001  6.847049395661e-002 -3.537762509466e-002  6.592975593456e-004  2.600733690373e-003  7.478976460177e-002 -1.488182269791e-002
  7.438370524663e-002 -1.650568516548e-002  6.663957537997e-004  2.723661634513e-003  5.641343731365e-002 -5.693035832892e-002 -2.070369894915e-001 -8.986367167361e-001
  3.380698172980e-004  2.715033111885e-003  7.497765935351e-002 -1.488546535615e-002 -2.063544808970e-001 -9.002700655374e-001  6.856095801756e-002 -3.019606086420e-002
  4.829977376755e-002 -6.288238652440e-002 -4.923832497425e-001 -7.721510464035e-001  6.298956599590e-002 -3.938489680891e-002  1.125377257145e-003  1.921732299021e-003
-4.925547500023e-001 -7.726263821707e-001  6.163450406360e-002 -4.486265928179e-002  1.299644022342e-003  1.492436402394e-003  6.462146347807e-002 -3.736630924981e-002
  6.308085276969e-002 -3.947655302643e-002  1.386741613180e-003  1.653454474207e-003  4.393874455850e-002 -6.448913049207e-002 -4.992743919180e-001 -7.660808533046e-001
  1.280875740087e-003  1.936760526874e-003  6.482369657086e-002 -3.743006383763e-002 -4.995203164654e-001 -7.674804458241e-001  6.284893613667e-002 -4.132139739274e-002
```

Data from 50MHz to 15GHz in  
10MHz steps



```
1.49900000e+010 -1.884123481138e-001  3.522933794755e-001  9.493645552321e-004  2.735890006358e-004  2.939002692375e-002 -8.676465491258e-003 -2.207496924854e-004  1.236065259912e-004
  9.463443060684e-004  3.105615146344e-004 -1.742347383703e-001  4.813685271232e-002 -6.152705437030e-004  1.614752661571e-003  6.774475978813e-002  9.617239585695e-003
  2.953403898205e-002 -8.707827389646e-003 -6.226849675423e-004  1.637610280621e-003 -1.595766021694e-001  3.757605914955e-001 -1.809501624148e-004 -7.061855554470e-004
-2.613575703191e-004  1.368108929760e-004  6.788329666403e-002  9.551687705500e-003 -2.146293806886e-004 -7.363580847286e-004 -1.199804891859e-001  7.697336952293e-002
1.50000000e+010 -1.883176013184e-001  3.545614742110e-001  9.524680768441e-004 -5.404222971799e-005  2.935126165241e-002 -1.235086132268e-002 -1.616280086909e-004  2.3473368458649e-004
  1.039250921080e-003 -6.032017103742e-005 -1.649137634331e-001  4.966164587830e-002 -6.748937194262e-005  1.689652681670e-003  6.725041473699e-002  1.961009613152e-003
  2.959693594806e-002 -1.251203706381e-002 -2.927441863297e-005  1.747754847916e-003 -1.531702433245e-001  3.773014940454e-001 -3.769459376261e-004 -5.671620228005e-004
-2.089293612250e-004  2.303682313561e-004  6.740524959192e-002  1.672663579641e-003 -4.385850073691e-004 -5.810569604703e-004 -1.121319455376e-001  7.458173831411e-002
```

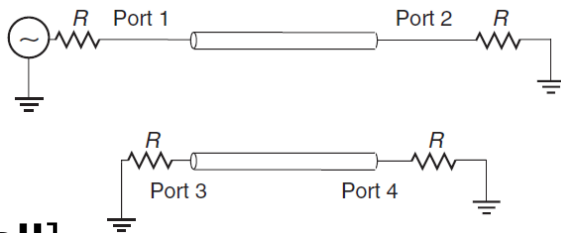


[Hall]

$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \\ b_4 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & S_{13} & S_{14} \\ S_{21} & S_{22} & S_{23} & S_{24} \\ S_{31} & S_{32} & S_{33} & S_{34} \\ S_{41} & S_{42} & S_{43} & S_{44} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ a_3 \\ a_4 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & S_{13} & S_{14} \\ S_{21} & S_{22} & S_{23} & S_{24} \\ S_{31} & S_{32} & S_{33} & S_{34} \\ S_{41} & S_{42} & S_{43} & S_{44} \end{bmatrix} \begin{bmatrix} v \\ 0 \\ -v \\ 0 \end{bmatrix}$$

$$S_{dd11} = \frac{b_{d1}}{a_{d1}} \bigg|_{a_2=a_4=0} = \frac{1}{2}(S_{11} + S_{33} - S_{13} - S_{31})$$

$$S_{dd21} = \frac{b_{d2}}{a_{d1}} \bigg|_{a_2=a_4=0} = \frac{1}{2}(S_{21} + S_{43} - S_{23} - S_{41})$$


# S-Parameter Channel Example

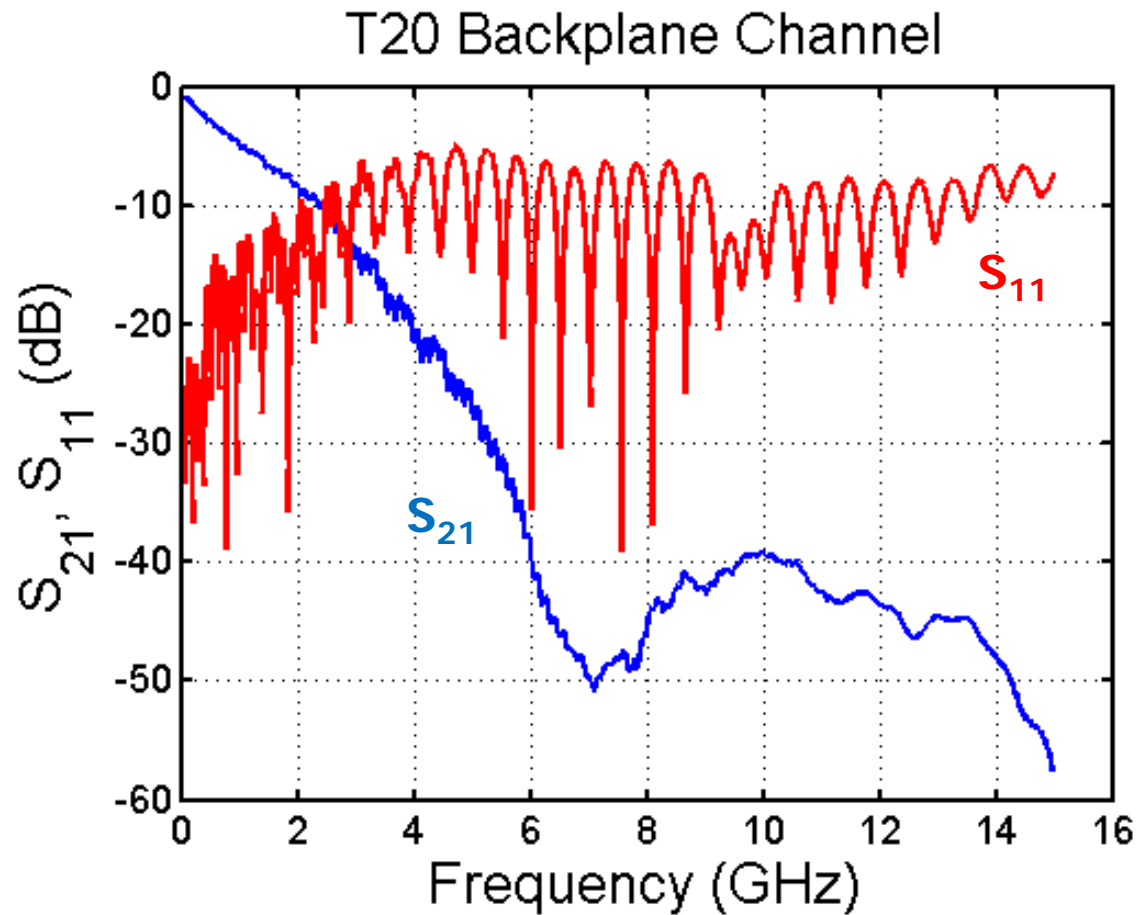
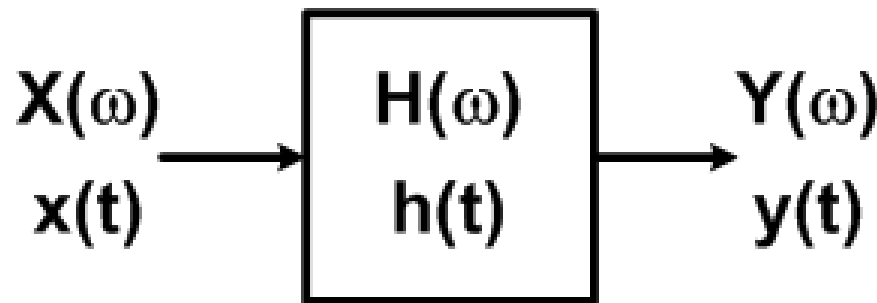
# Impulse Response

---

- Channel impulse responses are used in
  - Time domain simulations
  - Link analysis tools



$$Y(\omega) = H(\omega)X(\omega)$$

$$y(t) = h(t) * x(t) = \int_{-\infty}^{\infty} h(t - \tau)x(\tau) d\tau$$


$$h(t) = F^{-1}\{H(\omega)\}$$

# Generating an Impulse Response from S-Parameters

- Perform the inverse Fourier transform on the s-parameter of interest
- Step 1: For ifft, produce negative frequency values and append to s-parameter data in the following manner

$$S(-f) = S(f)^*$$

$$h(t) = F^{-1} \{S(\omega)\}$$

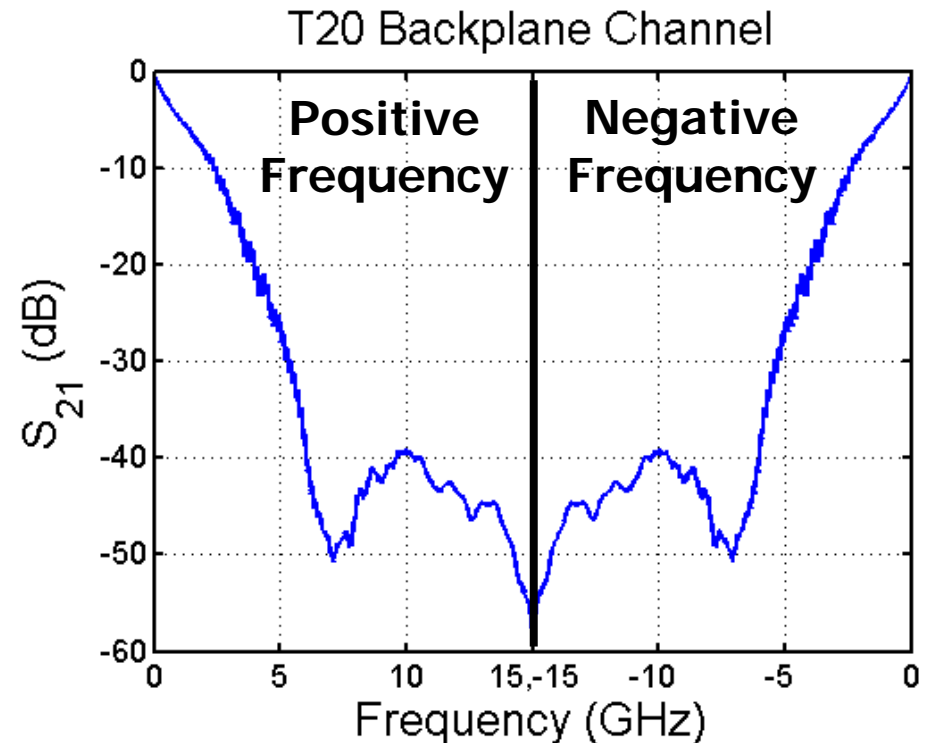


# Increasing Impulse Response Resolution

- Could perform ifft now, but will get an impulse response with time resolution of

$$\frac{1}{2f_{\max}} = \frac{1}{2(15\text{GHz})} = 33.3\text{ps}$$



- To improve impulse response resolution expand frequency axis and “zero pad”

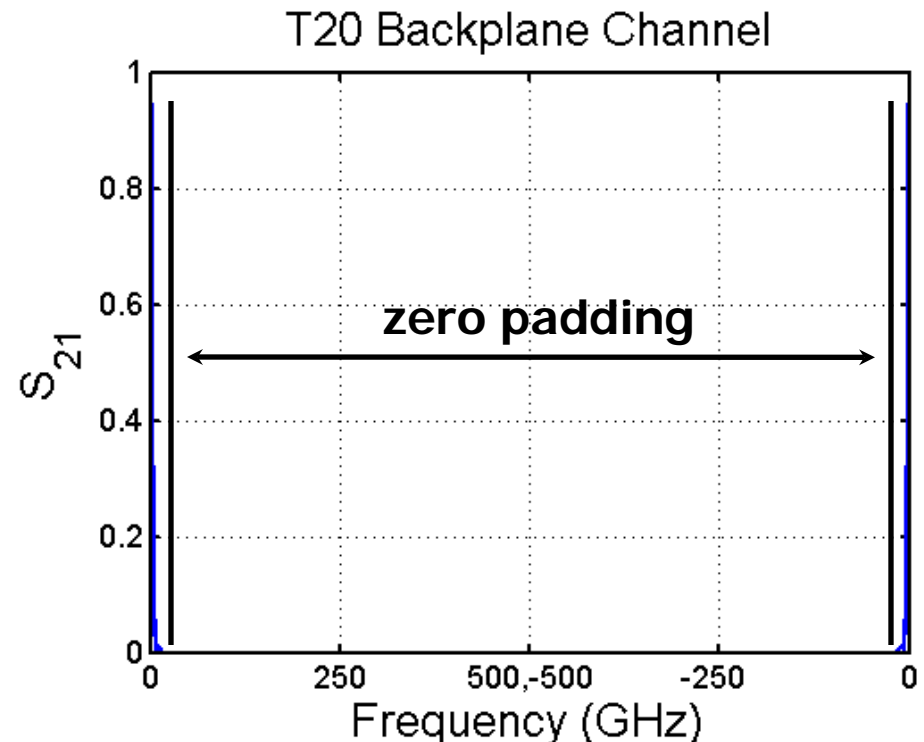For 1ps resolution:  
zero pad to +/-500GHz




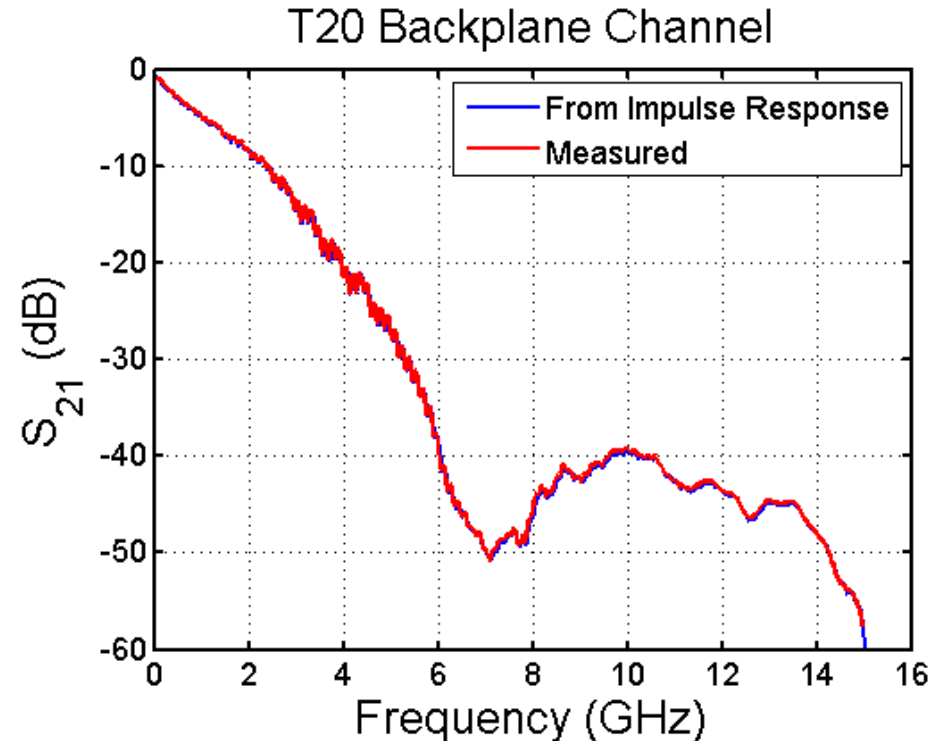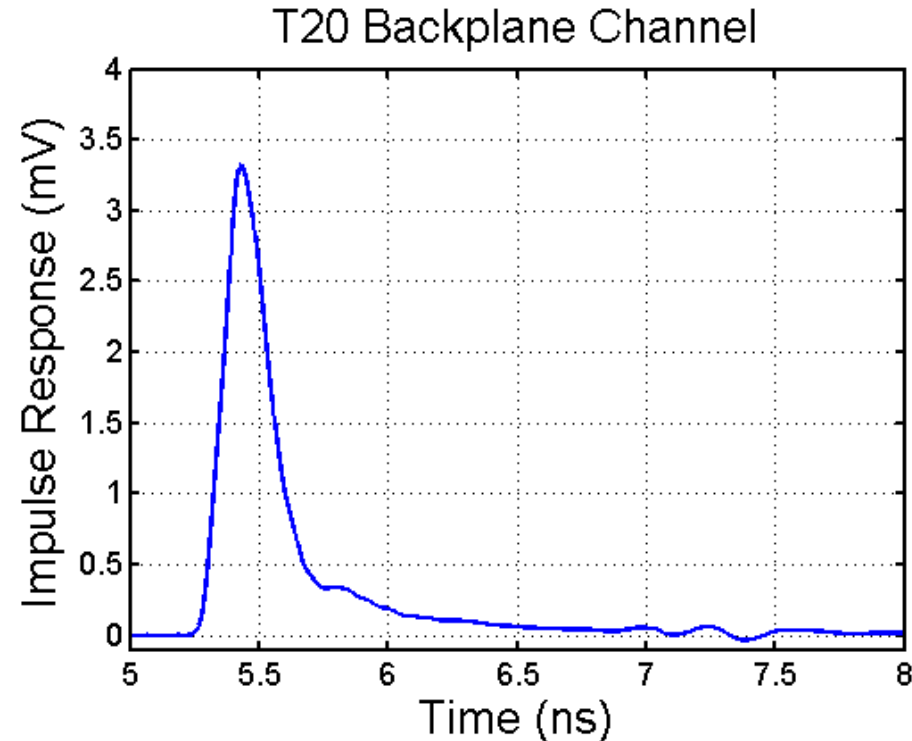
# Channel Impulse Response


- Now perform ifft to produce impulse response
- Can sanity check by doing an fft on impulse response and comparing to measured data



# Impulse Response of Different Channels


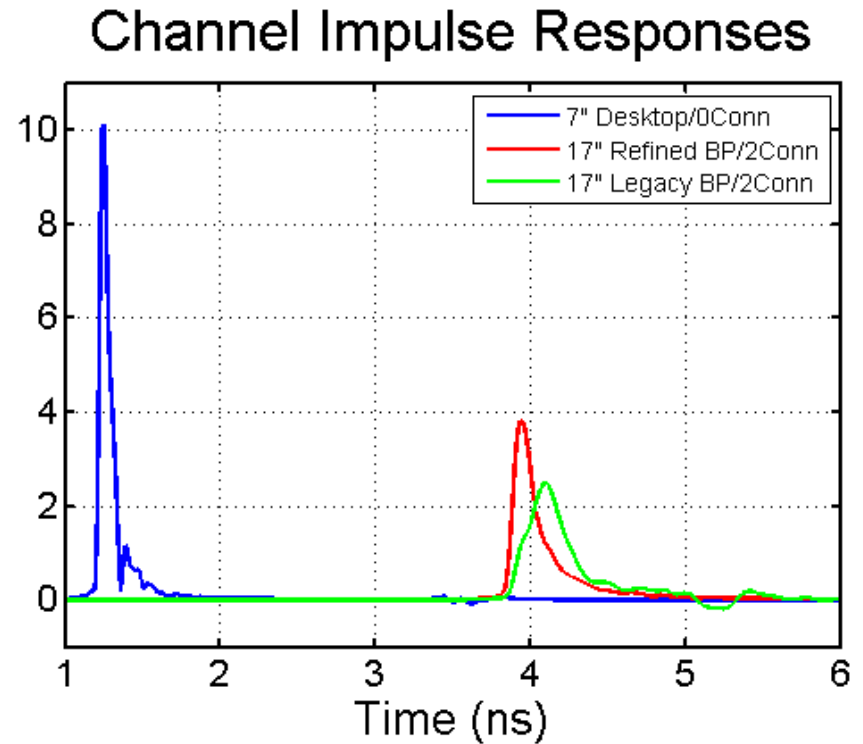
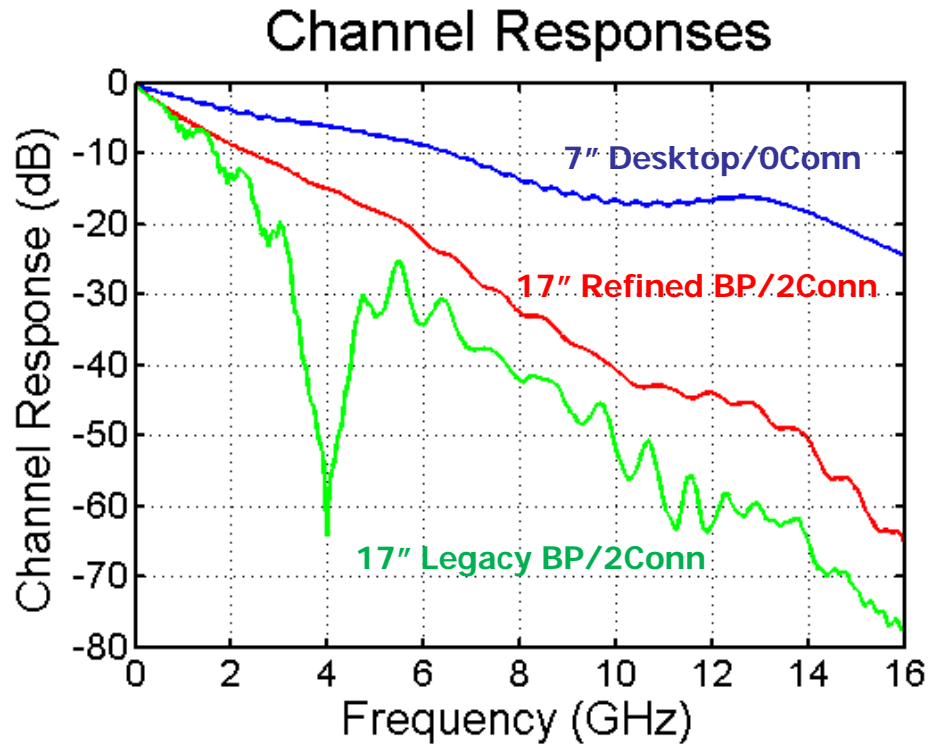


# Channel Transient Response

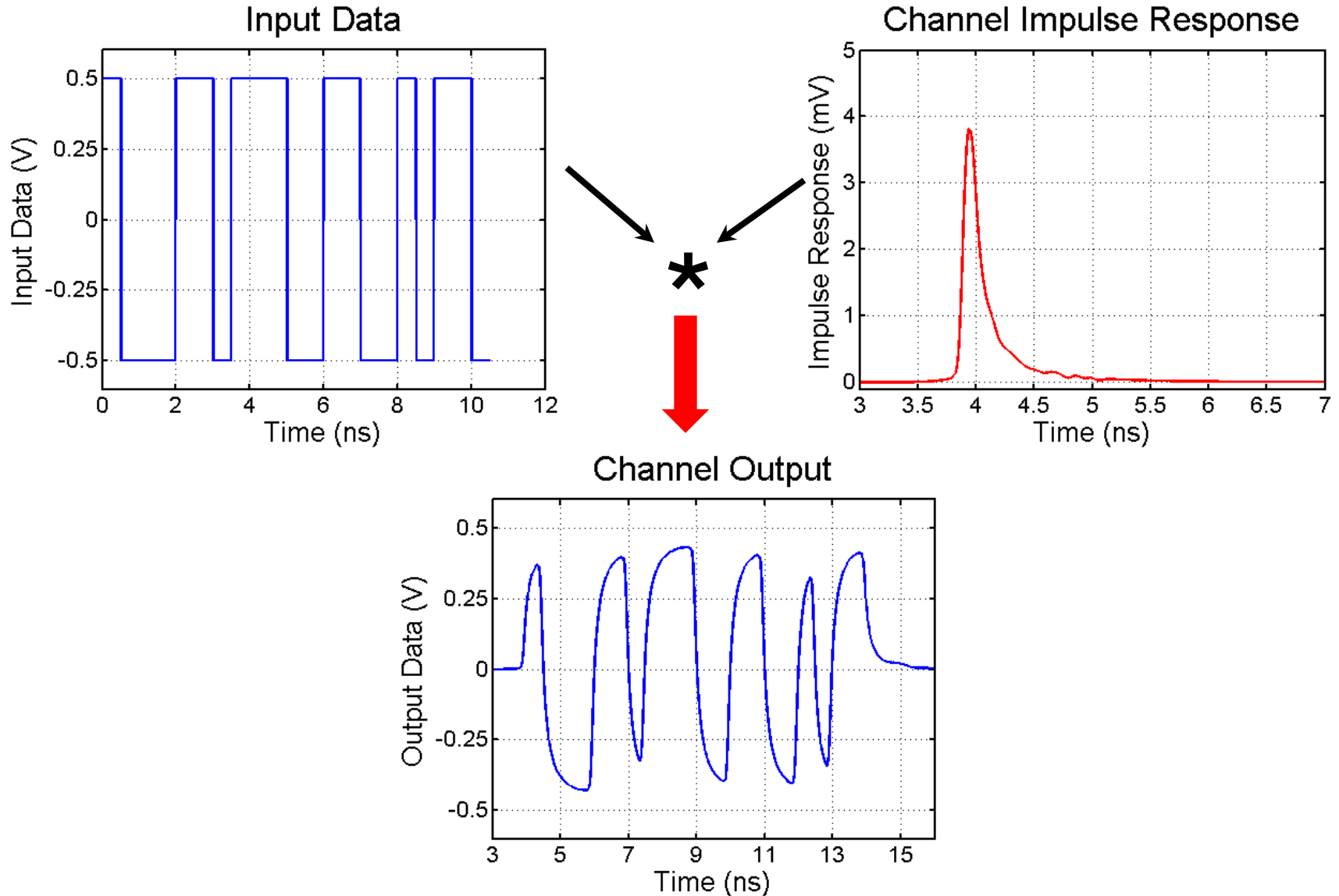




# Eye Diagrams

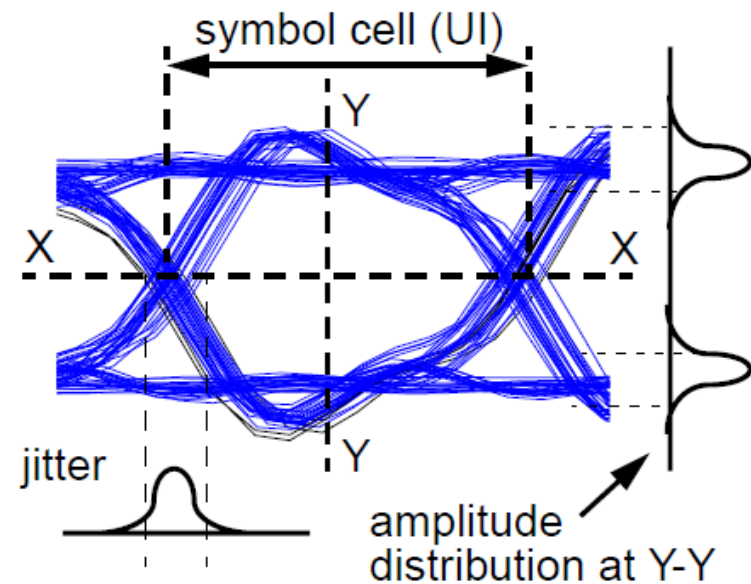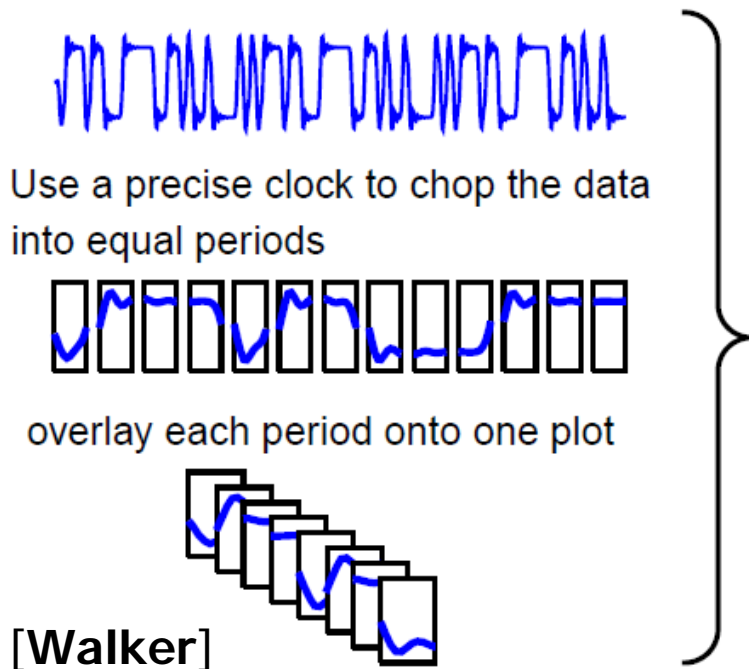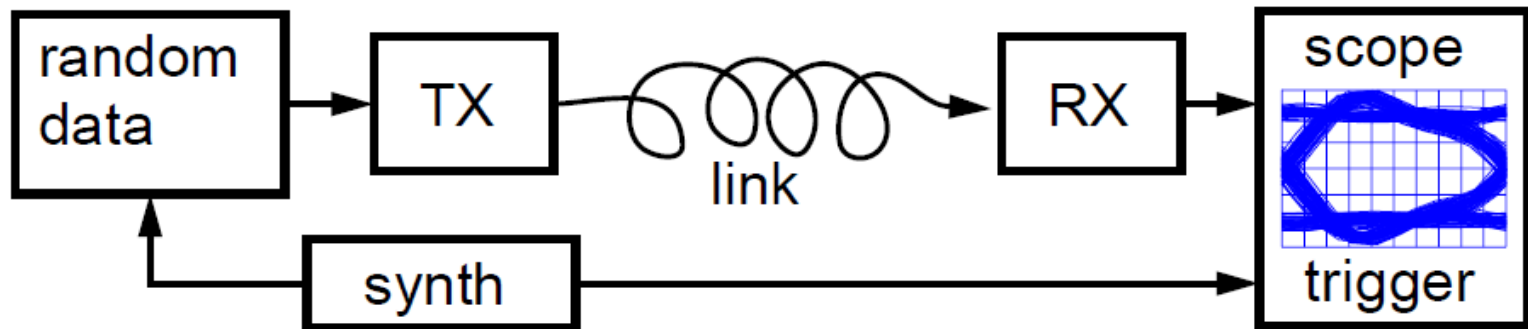


# Eye Diagrams vs Data Rate


Channel Frequency Response

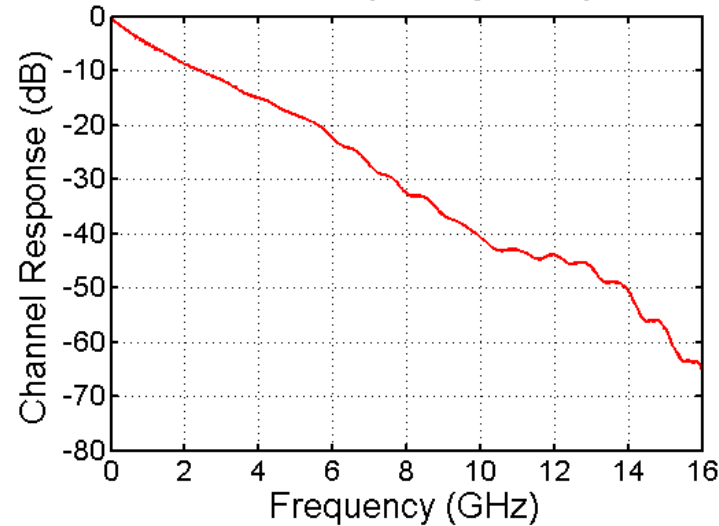


1Gb/s Eye

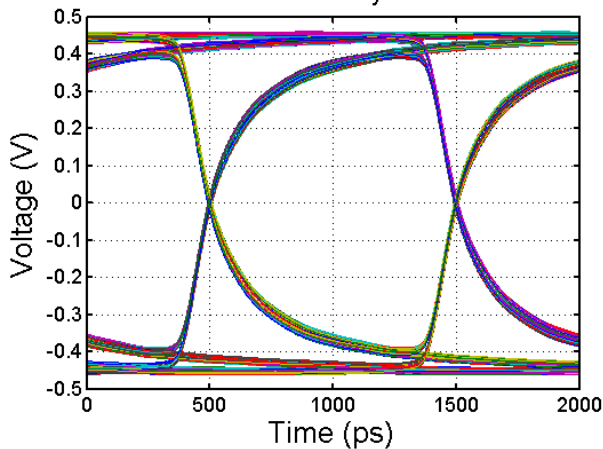





2Gb/s Eye

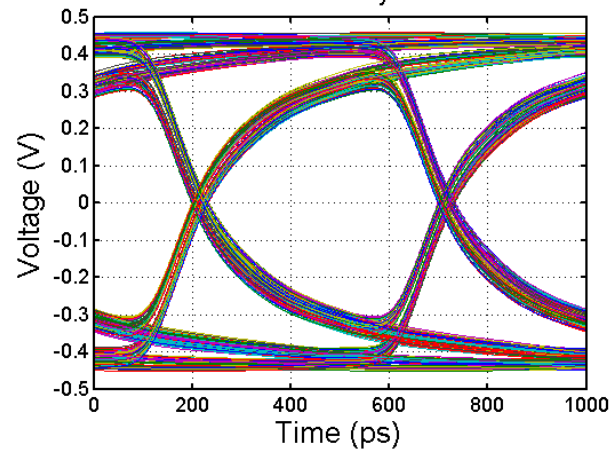

5Gb/s Eye

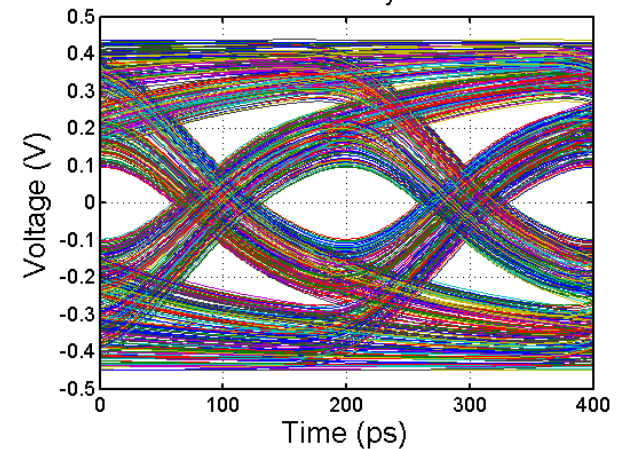


# Eye Diagrams vs Channel

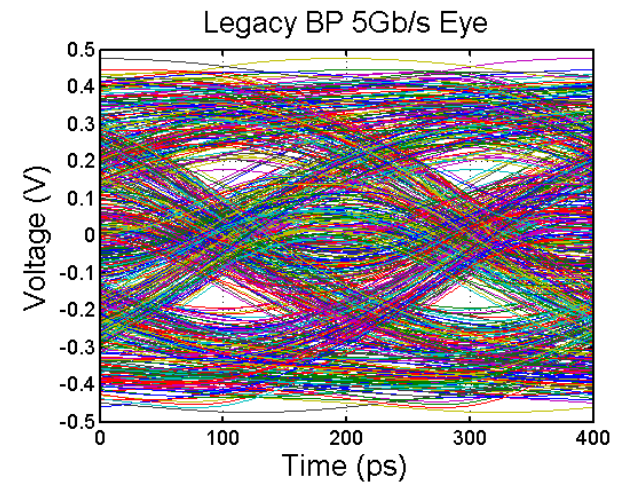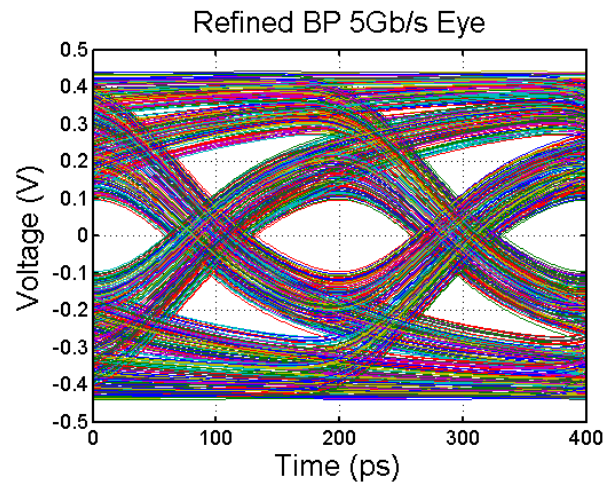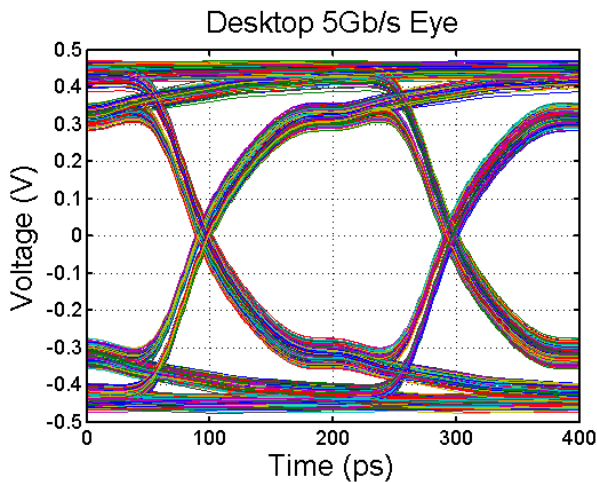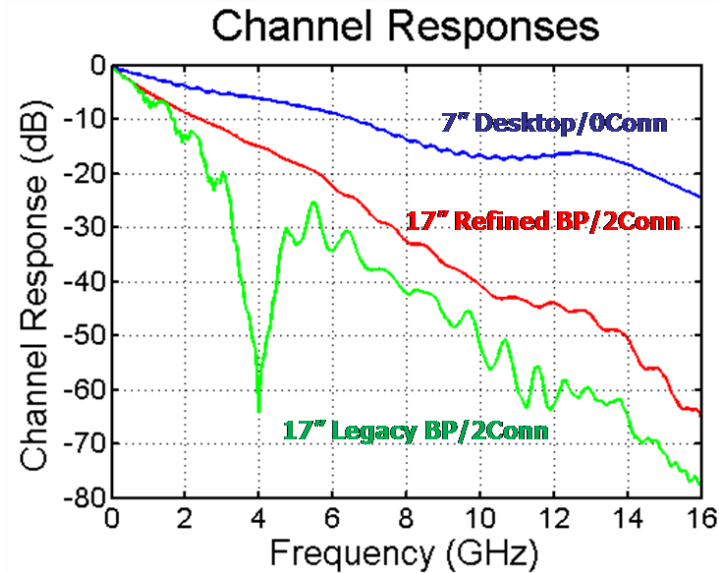


# Inter-Symbol Interference (ISI)

- Previous bits residual state can distort the current bit, resulting in inter-symbol interference (ISI)
- ISI is caused by
  - Reflections, Channel resonances, Channel loss (dispersion)

Legacy BP 5Gb/s Pulse Response

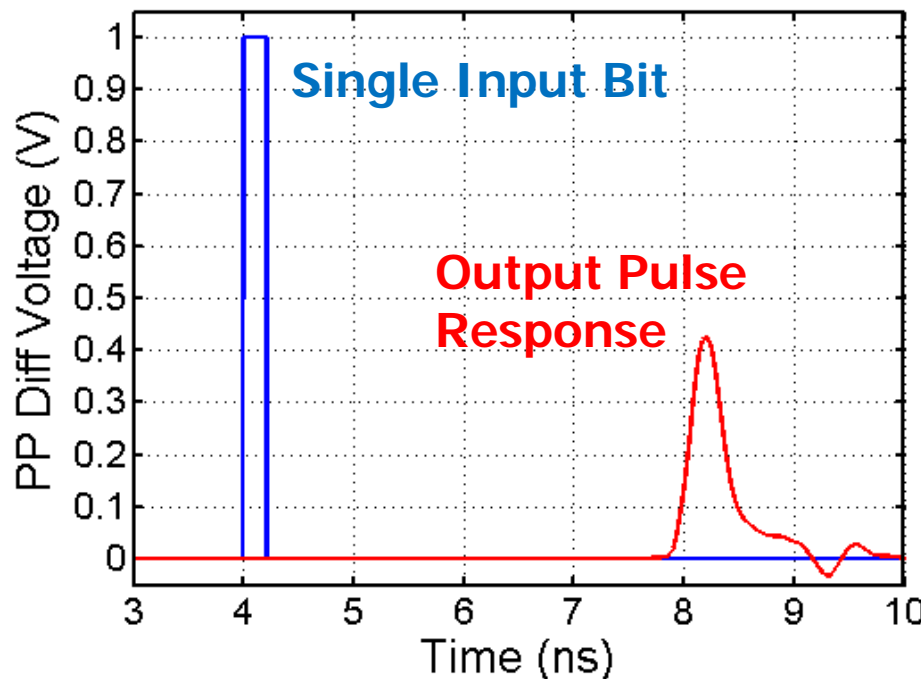


Legacy BP 5Gb/s Pulse Response

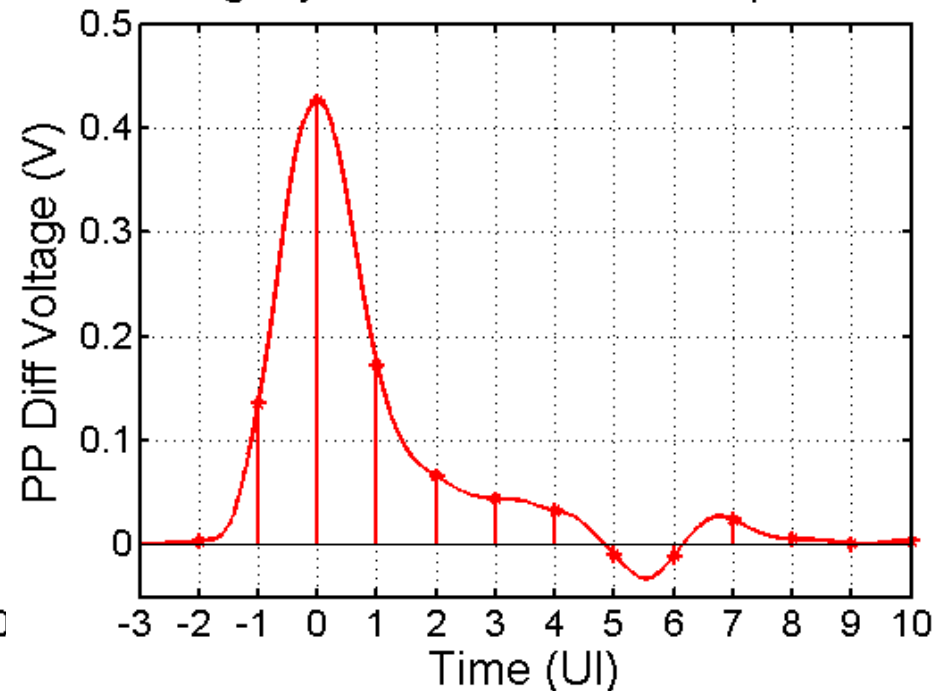
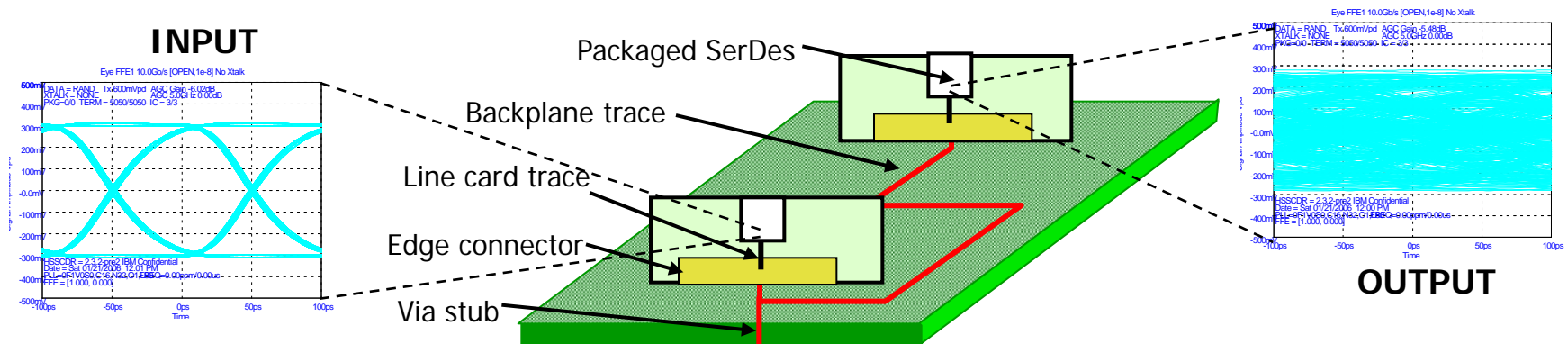
# ISI Impact

- At channel input (TX output), eye diagram is wide open
- As data pulses propagate through channel, they experience dispersion and have significant ISI
  - Result is a closed eye at channel output (RX input)



[Meghelli (IBM) ISSCC 2006]

# Next Time

---

- Channel pulse response model
- Modulation schemes